

PK 4

1.1) $U_q = 5V$

$$U_{CE} = 2,5V$$

$$R_c = 120 \Omega$$

$$I_B = 545 \mu A \quad \checkmark$$

$$I_c = 21,6 \text{ mA} \quad \checkmark$$

$$B = \frac{I_c}{I_B} = \underline{\underline{39,6}} \quad \checkmark$$

1.2) $I_{cx} = \frac{U_q - U_{CEX}}{R_c} = \frac{5V - 0,2V}{120 \Omega} = \underline{\underline{40 \text{ mA}}} \quad \checkmark$

$$I'_B = \frac{I_{cx}}{B} = \frac{40 \text{ mA}}{39,6} = \underline{\underline{1,01 \text{ mA}}}$$

$$I_{Bx} = m \cdot I'_B = 2 \cdot 1,01 \text{ mA} = \underline{\underline{2,02 \text{ mA}}}$$

$$R_2 = \frac{U_q - U_{BEK}}{I_{Bx}} = \frac{5V - 0,7V}{2,02 \text{ mA}} = \underline{\underline{2,13 \text{ k}\Omega}} \quad \checkmark$$

1.3) $R_c = 120 \Omega$

$$I_{Bx} = 2,02 \text{ mA}$$

$$I_{cx} = 39,4 \text{ mA}$$

$$U_{CEX} = 0,168 V$$

$$U_{BEK} = 0,77 V$$


$$R_2 = 2 \text{ k}\Omega$$

$$R_2 = \frac{U_q - U_{BEK}}{I_{Bx}} = \underline{\underline{2016,2 \Omega}} \quad \checkmark$$

Abweichung durch: Kabelwiderstand, ungenaue Messgeräte


1.4)

I_B [mA]	U_{CE} [V]
0,10	4,70
0,20	4,24
0,30	3,78
0,50	2,74
0,75	1,47
1,00	0,38
1,25	0,27
1,50	0,24
1,75	0,23
2,00	0,21

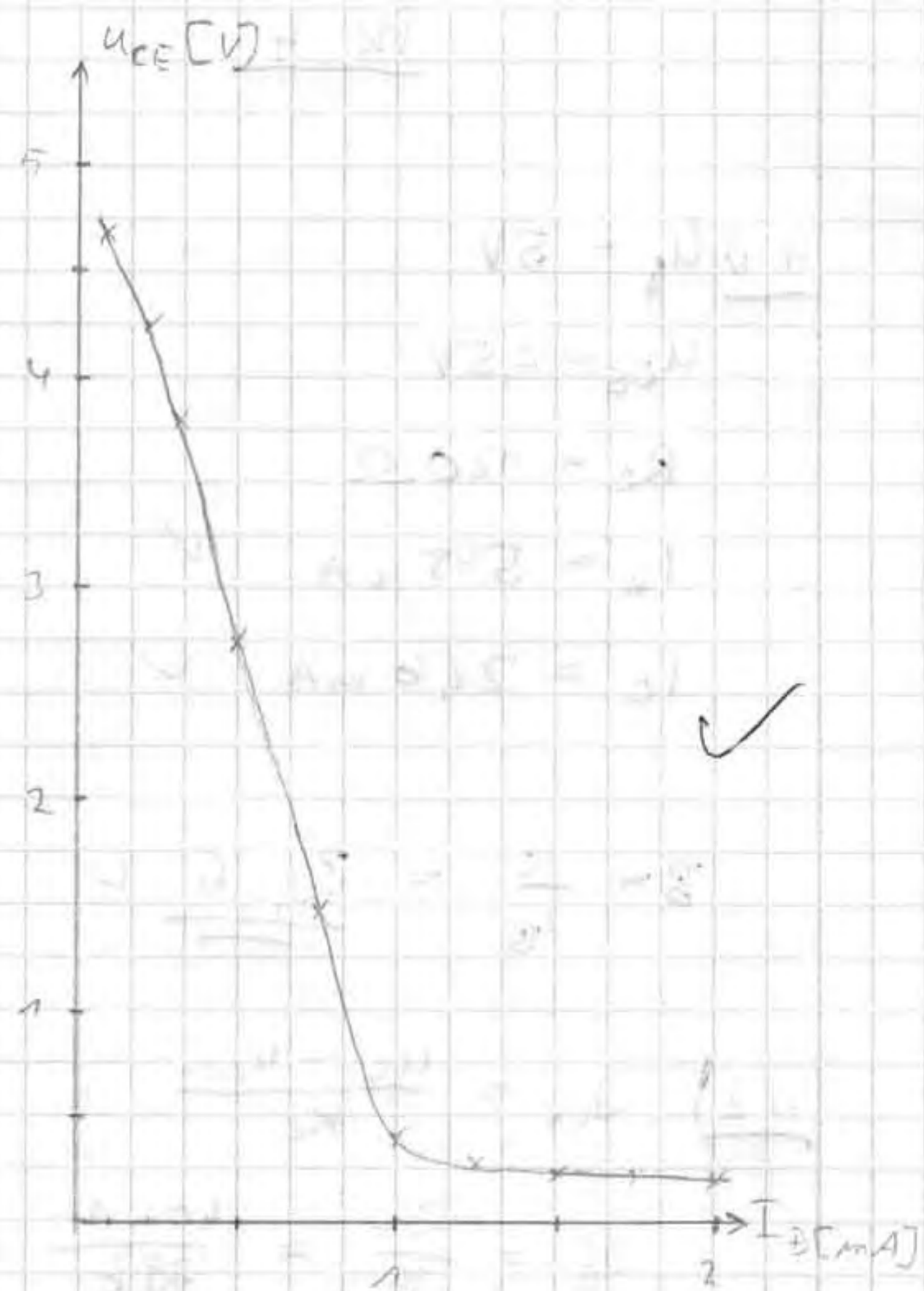


1.5)

U_e [V]	U_a [V]
0,15	4,48
0,25	4,44
0,50	4,39
0,75	4,30
1,00	4,19
1,25	3,93
1,30	1,19
1,35	1,04
1,40	0,84
1,50	0,70
ab 1,60	0,10

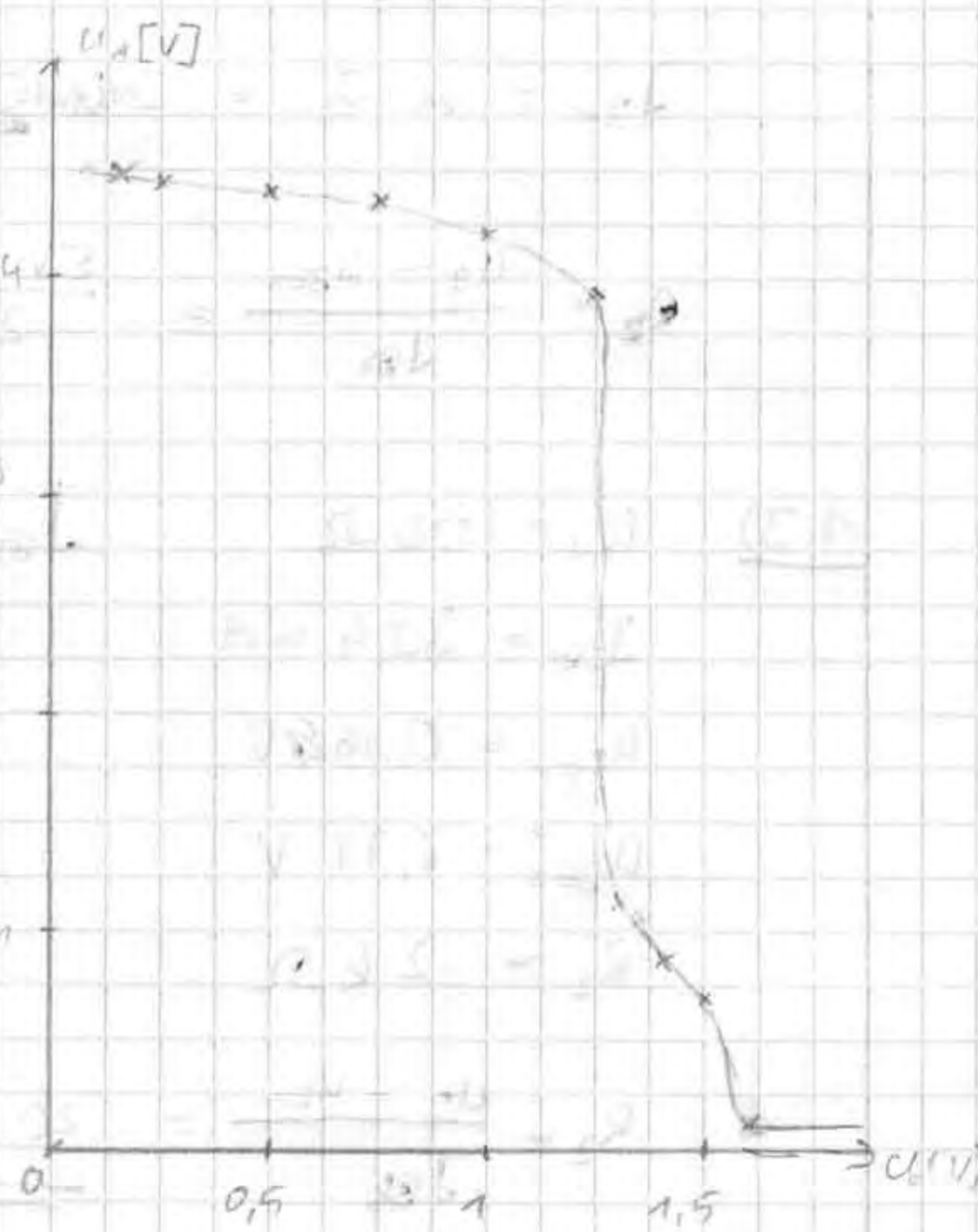

verbotener Bereich!

2.1)

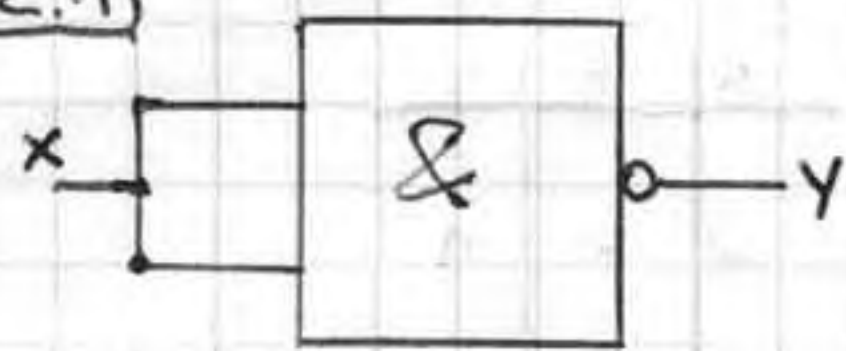

$$x = \bar{y}$$

$$U_{L, \text{Eingang}} = 0 \text{ V}$$

$$U_{H, \text{Eingang}} = 5,09 \text{ V}$$


x	y
0	1
1	0

L

$$0 \hat{=} U_{L, \text{Ausgang}} = 0,08 \text{ V}$$

$$1 \hat{=} U_{H, \text{Ausgang}} = 3,91 \text{ V}$$

2.2) a)

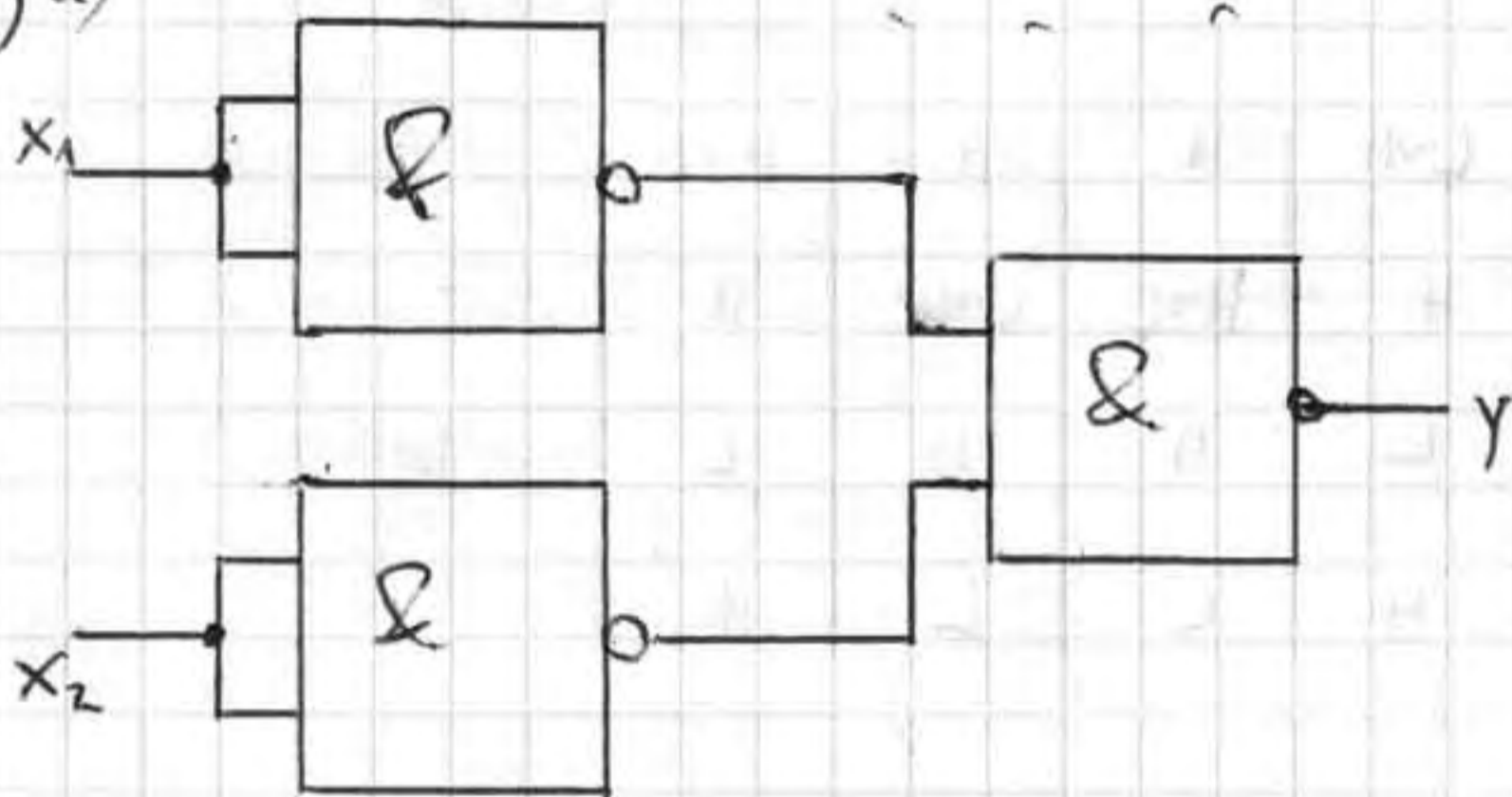


x ₁	x ₂	y
L	L	L
L	H	H
H	L	H
H	H	H

$$U_{H, \text{Ausgang}} = 3,91 \text{ V}$$

L

~~2.2) b)~~ b)

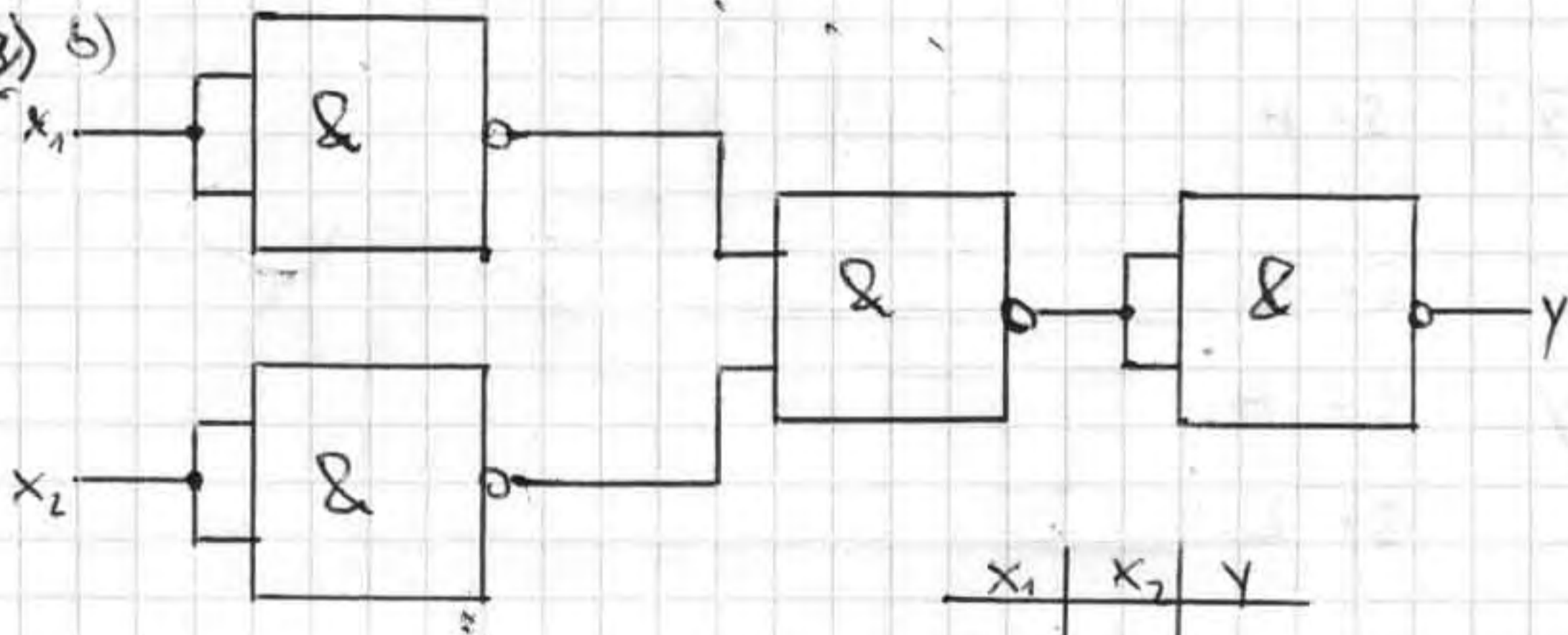


x ₁	x ₂	y
L	L	H
L	H	L
H	L	L
H	H	L

$$U_{H, \text{Ausgang}} = 3,91 \text{ V}$$

∴

✓

2.3) $y = a + \bar{b}$

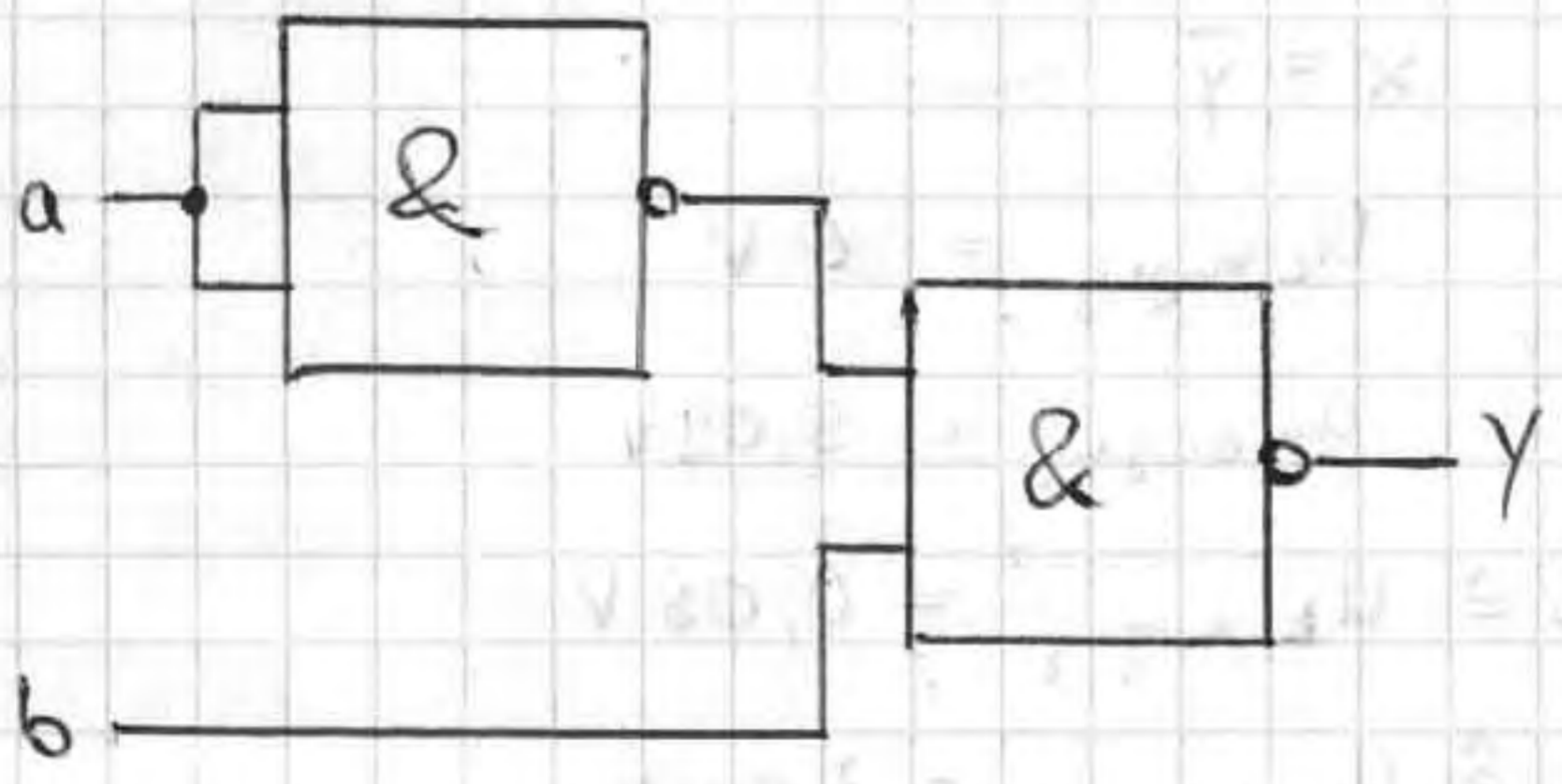

a	b	y
0	0	1
1	0	1
0	1	0
1	1	1

$U_{H, \text{Ausgang}} = 3,91 \text{ V}$

3.1)

R	L	L → H	H	H	H → L
S	H	H	H → L	L → H	H
Q	L	L	H	H	L
Q	H	H	L	L	H

3.2)


$R = 220 \Omega$

$C = 1,0 \mu\text{F}$

$f \approx \frac{1}{2 \cdot R \cdot C} = 2,3 \text{ kHz}$

für \bar{y} :
 $S = H \rightarrow \bar{y} = \text{Takt}$
 $S = L \rightarrow \text{kein Takt}$

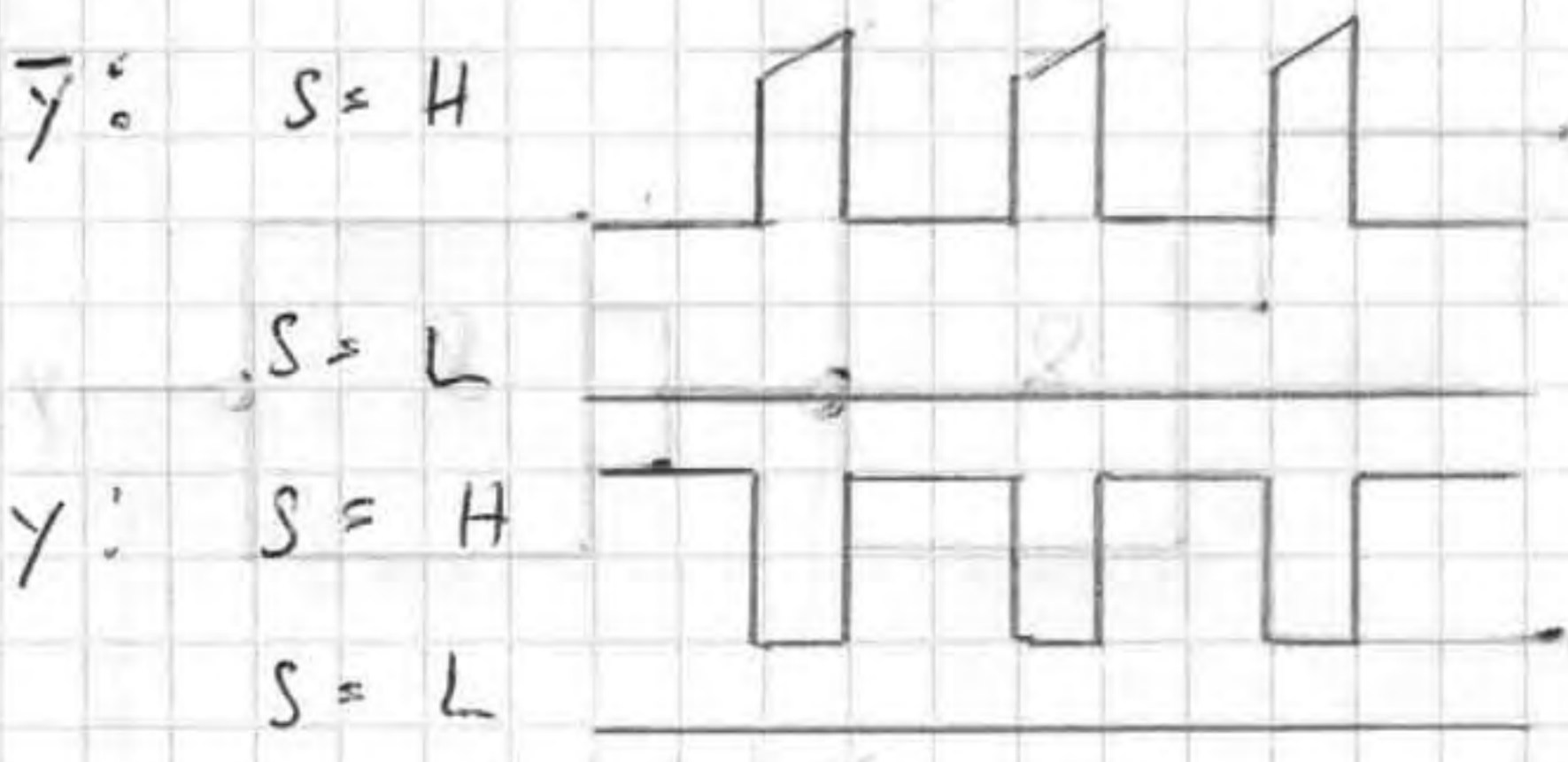für y :
 $S = H \rightarrow \text{Takt}$
 $S = L \rightarrow \text{kein Takt}$



3.3) für $x_1 = \text{Takt}$

$x_2 = \text{high}$

$y = \text{Takt}$

mit $x_2 = 1$

$x_1 = \text{Takt}$

$x_2 = \text{high}$

$y = \text{Takt}$

$x_1 = \text{Takt}$

$x_2 = \text{Low}$

$y = \text{kein Takt}$

3.4) $t_i = R \cdot C$

$R = 10 \text{ k}\Omega$

$C = 470 \mu\text{F}$

$t_i = 10 \text{ k}\Omega \cdot 470 \mu\text{F}$

$t_i = 4,7 \text{ s}$

4.1

E_1	E_2	E_3	A
0	0	0	1
1	0	0	1
0	1	0	1
1	1	0	1
0	0	1	1
1	0	1	1
0	1	1	1
1	1	1	0

U_A für 0: 0,18V

1: 4,48V

$E_1 \wedge E_2 \wedge E_3 = A$

